



# **ST. XAVIER'S COLLEGE**

## **DEPARTMENT OF COMPUTER SCIENCE**

MAITIGHAR, KATHMANDU, NEPAL

| <http://www.sxc.edu.np> | [sxc\\_cs@sxc.edu.np](mailto:sxc_cs@sxc.edu.np) |



### **Digital Logic Lab Assignment # 1**

1. To verify the operation of Derived Gates.

#### **Submitted By**

Name

Year/SEM

Roll No.

#### **Submitted To**

	Signature	Remarks
Er. Rajan Karmacharya Lecturer, Dept. of Computer Science		
Er. Saugat Sigdel Lecturer, Dept. of Computer Science		
Mr. Ganesh Dhami Lecturer, Dept. Of Computer Science		

## DL LAB ASSIGNMENT #1

### OBJECTIVE 1.1:


TO VERIFY THE OPERATION OF NOR GATE.

### THEORY:

NOR gate can be defined as the combination of OR gate and NOT gate. In other words output of OR gate is connected to the input of NOT gate. Note that output of OR gate is inverted to form NOR gate.

**Boolean expression's= (A+B)**


### CIRCUIT DIAGRAM:

 

### TRUTH TABLE:

INPUTS		OUTPUT
A	B	(A+B)'
0	0	1
0	1	0
1	0	0
1	1	0

### OBSERVATION:

 

## DL LAB ASSIGNMENT #1

### OBSERVATION TABLE:

INPUTS		OUTPUT
A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0

### CONCLUSION:

Hence, the logical operation of NOR gate was verified.

### REFERENCE:

<http://www.physicshandbook.com/topic/topiccc/comb gates.htm>

## DL LAB ASSIGNMENT #1

### OBJECTIVE 1.2:


TO VERIFY OPERATION OF NOR GATE.

### THEORY:

Combination of AND gate NOT gate results in the formation of NAND gate as shown in fig below. Here in this gate output is opposite of the AND gate and output of AND gate is connected to the input of NOT gate.

**Boolean expression:  $F=(A.B)'$**

### CIRCUIT DIAGRAM:

 

### TRUTH TABLE:

INPUTS		OUTPUT
A	B	$(A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

### OBSRVATION:

## DL LAB ASSIGNMENT #1

 


Fig: Logical operation of NAND gate

### OBSERVATION TABLE:

INPUTS		OUTPUT
A	B	$(A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

### CONCLUSION:

Hence, the property of NAND gate was verified.

### REFERENCE:

<http://www.physicshandbook.com/topic/topiccc/combgates.htm>